

## **EXPERIMENT: 1                      LOGIC GATES**

AIM: To study and verify the truth table of logic gates

LEARNING OBJECTIVE:

- Identify various ICs and their specification.

COMPONENTS REQUIRED:

- Logic gates (IC) trainer kit.
- Connecting patch chords.
- IC 7400, IC 7408, IC 7432, IC 7406, IC 7402, IC 7404, IC 7486

THEORY:

The basic logic gates are the building blocks of more complex logic circuits. These logic gates perform the basic Boolean functions, such as AND, OR, NAND, NOR, Inversion, Exclusive-OR, Exclusive-NOR. Fig. below shows the circuit symbol, Boolean function, and truth. It is seen from the Fig that each gate has one or two binary inputs, A and B, and one binary output, C. The small circle on the output of the circuit symbols designates the logic complement. The AND, OR, NAND, and NOR gates can be extended to have more than two inputs. A gate can be extended to have multiple inputs if the binary operation it represents is commutative and associative.

These basic logic gates are implemented as small-scale integrated circuits (SSICs) or as part of more complex medium scale (MSI) or very large-scale (VLSI) integrated circuits. Digital IC gates are classified not only by their logic operation, but also the specific logic-circuit family to which they belong. Each logic family has its own basic electronic circuit upon which more complex digital circuits and functions are developed. The following logic families are the most frequently used.

TTL → Transistor-transistor logic

ECL → Emitter-coupled logic

MOS → Metal-oxide semiconductor

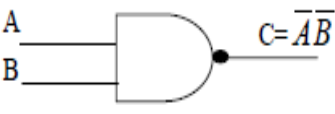
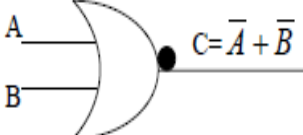

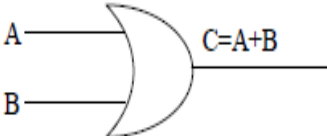
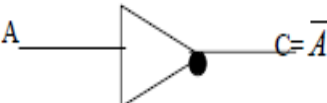
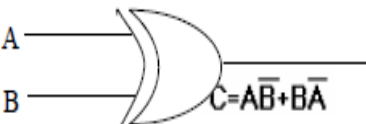
CMOS → Complementary metal-oxide semiconductor

TTL and ECL are based upon bipolar transistors. TTL has a well established popularity among logic families. ECL is used only in systems requiring high-speed operation. MOS and CMOS, are based on field effect transistors. They are widely used in large scale integrated circuits because of their high component density and relatively low power consumption. CMOS logic consumes far less power than MOS logic. There are various commercial

integrated circuit chips available. TTL ICs are usually distinguished by numerical designation as the 5400 and 7400 series.

**PROCEDURE:**

1. Check the components for their working.
2. Insert the appropriate IC into the IC base.
3. Make connections as shown in the circuit diagram.
4. Provide the input data via the input switches and observe the output on output LEDs

S.NO	GATE	SYMBOL	INPUTS		OUTPUT
			A	B	
1.	NAND IC 7400	 $C = \overline{AB}$	0	0	1
			0	1	1
			1	0	1
			1	1	0
2.	NOR IC 7402	 $C = \overline{A+B}$	0	0	1
			0	1	0
			1	0	0
			1	1	0
3.	AND IC 7408	 $C = AB$	0	0	0
			0	1	0
			1	0	0
			1	1	1
4.	OR IC 7432	 $C = A+B$	0	0	0
			0	1	1
			1	0	1
			1	1	1
5.	NOT IC 7404	 $C = \overline{A}$	1	-	0
			0	-	1
6.	EX-OR IC 7486	 $C = A\overline{B} + \overline{A}B$	0	0	0
			0	1	1
			1	0	1
			1	1	0

**VIVA QUESTIONS:**

1. Why NAND & NOR gates are called universal gates?
2. Realize the EX – OR gates using minimum number of NAND gates.
3. Give the truth table for EX-NOR and realize using NAND gates?
4. What are the logic low and High levels of TTL IC's and CMOS IC's?
5. Compare TTL logic family with CMOS family?
6. Which logic family is fastest and which has low power dissipation?

**EXPERIMENT: 2      REALIZATION OF A BOOLEAN FUNCTION.**

**AIM:** To simplify the given expression and to realize it using Basic gates and Universal gates

**LEARNING OBJECTIVE:**

- To simplify the Boolean expression and to build the logic circuit.
- Given a Truth table to derive the Boolean expressions and build the logic circuit to realize it.

**COMPONENTS REQUIRED:**

IC 7400, IC 7408, IC 7432, IC 7406, IC 7402, Patch Cords & IC Trainer Kit.

**THEORY:**

*Canonical Forms (Normal Forms):* Any Boolean function can be written in disjunctive normal form (sum of min-terms) or conjunctive normal form (product of max-terms).

A Boolean function can be represented by a Karnaugh map in which each cell corresponds to a minterm. The cells are arranged in such a way that any two immediately adjacent cells correspond to two minterms of distance 1. There is more than one way to construct a map with this property.

**Karnaugh Maps**

For a function of two variables, say,  $f(x, y)$ ,

	$x'$	$x$
$y'$	$f(0,0)$	$f(1,0)$
$y$	$f(0,1)$	$f(1,1)$

For a function of three variables, say,  $f(x, y, z)$

	$x'y'$	$x'y$	$xy$	$xy'$
$z'$	$f(0,0,0)$	$f(0,1,0)$	$f(1,1,0)$	$f(1,0,0)$
$z$	$f(0,0,1)$	$f(0,1,1)$	$f(1,1,1)$	$f(1,0,1)$

For a function of four variables:  $f(w, x, y, z)$

	w'x'	w'x	wx	wx'
y'z'	0	4	12	8
y'z	1	5	13	9
yz	3	7	15	11
yz'	2	6	14	10

Realization of Boolean expression:


$$1) \quad Y = \bar{A}\bar{B}C\bar{D} + \bar{A}BC\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D}$$

AB

			1
			1
			1
1	1	1	1

After simplifying using K-Map method we get  $Y = A\bar{B} + C\bar{D}$


Realization using Basic gates

 


TRUTH TABLE

INPUTS				OUTPUT
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Realization using NAND gates

 

Realization using NOR gates

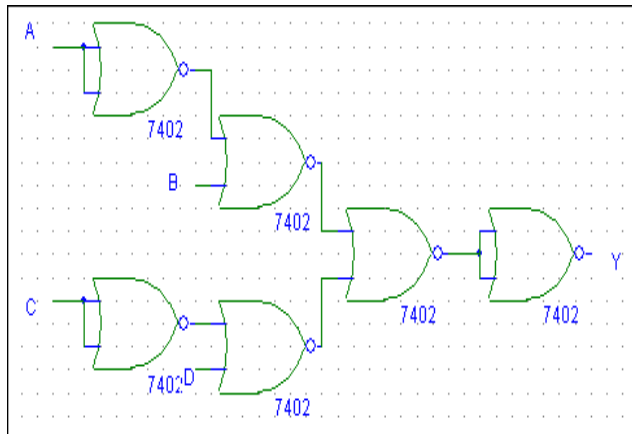

2) For the given Truth Table, realize a logical circuit using basic gates and NAND gates

Inputs				Output
A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

#### PROCEDURE:

Check the components for their working.

Insert the appropriate IC into the IC base.

Make connections as shown in the circuit diagram.

Provide the input data via the input switches and observe the output on output LEDs

Verify the Truth Table

RESULT: Simplified and verified the Boolean function using basic gates and universal gates

#### VIVA QUESTIONS:

- 1) What are the different methods to obtain minimal expression?
- 2) What is a Min term and Max term
- 3) State the difference between SOP and POS.

- 4) What is meant by canonical representation?
- 5) What is K-map? Why is it used?
- 6) What are universal gates?

### EXPERIMENT: 3          ADDERS AND SUBTRACTORS

AIM: To realize

- i) Half Adder and Full Adder
- ii) Half Subtractor and Full Subtractor by using Basic gates and NAND gates

LEARNING OBJECTIVE:

- To realize the adder and subtractor circuits using basic gates and universal gates
- To realize full adder using two half adders
- To realize a full subtractor using two half subtractors

COMPONENTS REQUIRED:

IC 7400, IC 7408, IC 7486, IC 7432, Patch Cords & IC Trainer Kit.

THEORY:

*Half-Adder:* A combinational logic circuit that performs the addition of two data bits, A and B, is called a half-adder. Addition will result in two output bits; one of which is the sum bit, S, and the other is the carry bit, C. The Boolean functions describing the half-adder are:

$$S = A \oplus B \qquad C = A B$$

*Full-Adder:* The half-adder does not take the carry bit from its previous stage into account. This carry bit from its previous stage is called carry-in bit. A combinational logic circuit that adds two data bits, A and B, and a carry-in bit, Cin, is called a full-adder. The Boolean functions describing the full-adder are:

$$S = (x \oplus y) \oplus \text{Cin} \qquad C = xy + \text{Cin} (x \oplus y)$$

*Half Subtractor:* Subtracting a single-bit binary value B from another A (i.e. A - B) produces a difference bit D and a borrow out bit B-out. This operation is called half subtraction and the circuit to realize it is called a half subtractor. The Boolean functions describing the half-Subtractor are:


$$S = A \oplus B \qquad C = A' B$$

*Full Subtractor:* Subtracting two single-bit binary values, B, Cin from a single-bit value A produces a difference bit D and a borrow out Br bit. This is called full subtraction. The Boolean functions describing the full-subtractor are:

$$D = (x \oplus y) \oplus \text{Cin} \qquad \text{Br} = A' B + A' (\text{Cin}) + B(\text{Cin})$$


**I. TO REALIZE HALF ADDER****TRUTH TABLE**

INPUTS		OUTPUTS	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 **i) Basic Gates****BOOLEAN EXPRESSIONS:**

$$S = A \oplus B$$

$$C = A B$$

 **ii) NAND Gates****II. FULL ADDER****TRUTH TABLE**


INPUTS			OUTPUTS	
A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**BOOLEAN EXPRESSIONS:**


$$S = A \oplus B \oplus C$$

$$C = A B + B C_{in} + A C_{in}$$

**i) BASIC GATES**

 

## ii) NAND GATES

 

## III. HALF SUBTRACTOR

### TRUTH TABLE



INPUTS		OUTPUTS	
A	B	D	Br
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

### BOOLEAN EXPRESSIONS:

$$D = A \oplus B$$

$$Br = \bar{A}B$$

 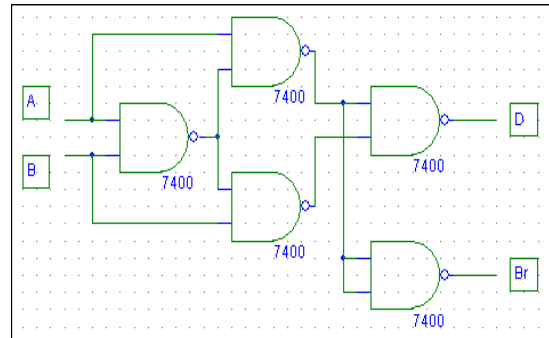


**i) BASIC GATES****ii) NAND Gates****IV. FULL SUBTRACTOR****TRUTH TABLE**


INPUTS			OUTPUTS	
A	B	Cin	D	Br
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

**BOOLEAN EXPRESSIONS:**

$$D = A \oplus B \oplus C$$

$$Br = \bar{A} B + B Cin + \bar{A} Cin$$

 **i) BASIC GATES**

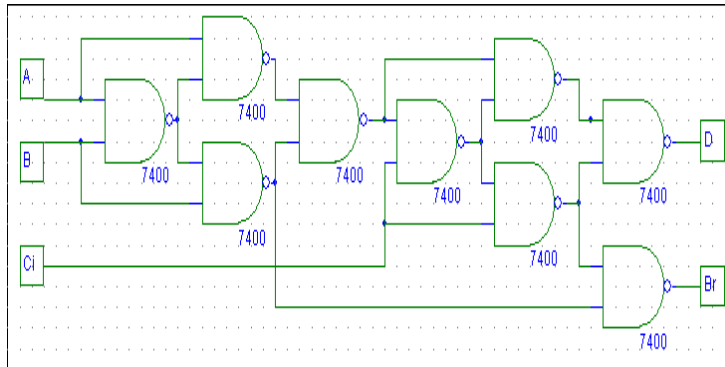**ii) To Realize the Full subtractor using NAND Gates only****PROCEDURE:**

- Check the components for their working.
- Insert the appropriate IC into the IC base.
- Make connections as shown in the circuit diagram.
- Verify the Truth Table and observe the outputs.

**RESULT:** The truth table of the above circuits is verified.

**VIVA QUESTIONS:**

- 1) What is a half adder?
- 2) What is a full adder?
- 3) What are the applications of adders?
- 4) What is a half subtractor?
- 5) What is a full subtractor?
- 6) What are the applications of subtractors?
- 7) Obtain the minimal expression for above circuits.
- 8) Realize a full adder using two half adders
- 9) Realize a full subtractors using two half subtractors